

Lab 8 - Motor Characterization

Jiaying Wei

November 2013

1 Introduction

Hmmm...hi, I'm Jiaying, and today I'm here to tell you how the electrical domain and the mechanical domain of our motor is related. I could put some stuffs about what I learned about this lab, but I think the sections below do a much better job than this intro could ever hope to do.

2 Prelab

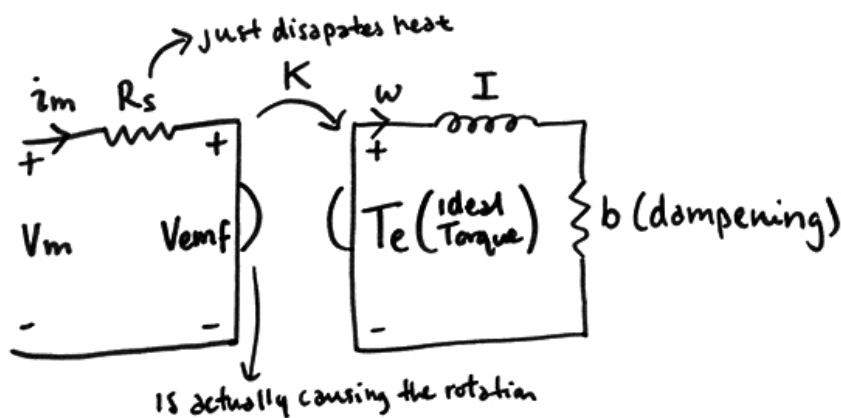


Figure 1: Electrical and mechanical domainssssss.

R_s or the motor series resistance, is the resistance the motor normally has without all that extra turning.

K or the motor constant, is how V_{emf} is related to T_e .

I or the moment of inertia, is how much our motor resist acceleration.

b or the linearized motor losses, is essentially dampening caused by the motor resisting movement cause it has a chunk of huge ass plastic mounted onto it.

3 Build time

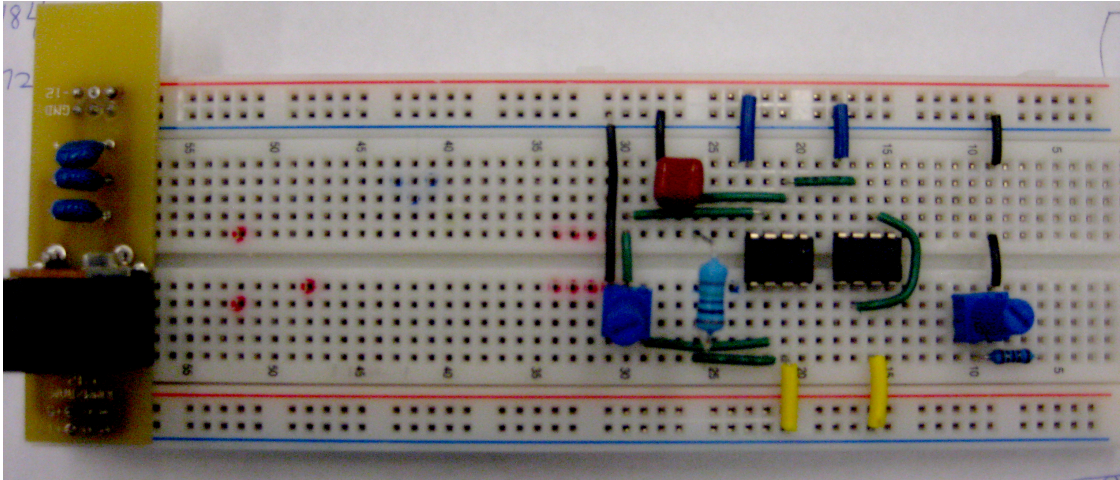


Figure 2: What I built.

4 Lab time

4.1 Series Resistance

I measured my series resistance which is the amount of resistance the motor has naturally without moving. It turns out $R_s = 22.9\Omega$

4.2 Motor Constant

Lower Voltage

Finding V_{emf}

$$R_s = 22.9\Omega$$

$$V_m = 1.30V$$

$$i_m = .0048A$$

$$V_{emf} = V_m - i_m R_s = 1.19V$$

Finding w (angular velocity)

$$Revolutions = 30$$

$$Totaltime = 28.327s$$

$$w = 6.65rad/s$$

Finding motor constant K

$$K = \frac{V_{emf}}{w} = 0.179V \cdot s$$

Higher Voltage

Finding V_{emf}

$$R_s = 22.9\Omega$$

$$V_m = 4.42V$$

$$i_m = .0041A$$

$$V_{emf} = V_m - i_m R_s = 4.42V$$

Finding w (angular velocity)

$$Revolutions = 30$$

$$Totaltime = 11.112s$$

$$w = 16.96rad/s$$

Finding motor constant K

$$K = \frac{V_{emf}}{w} = 0.26V \cdot s$$

My K values for my lower and higher V_{ins} are different, which Forest says is suppose to happen, so that's good. We will agree that V_{emf} is to T_e as i_m is to w . $\frac{V_{emf}}{i_m} = \frac{T_e}{w}$ and K is the proportionality constant, therefor it makes perfect sense that I use $V_{emf} = Kw$ in order to find my motor constant.

5 Time Constant

I found the time constant for the motor by taking the voltage of my motor from the oscilloscope. I would find the change in voltage in the motor and then take 63% of that. I would then search in my matrix for the first matching voltage, find the Δt from the original time.

$$\tau_{noload} = 0.484s$$

$$\tau_{loaded} = 5.372s$$

5.1 Motor losses and moment of inertia

So because we accept the truth that $\sum T = I\dot{w}$ (which totally is just the torque formula, remember w is just velocity so \dot{w} is acceleration).

$$V_{emf} = Kw$$

$$w = \frac{V_{emf}}{K}$$

$$\sum T = I\dot{w}$$

$$T_e = I\dot{w} + bw$$

$$Ki_m = \frac{I}{K} \dot{V_{emf}} + \frac{b}{K} V_{emf}$$

$$i_m = \frac{I}{K^2} \dot{V_{emf}} + \frac{b}{K^2} V_{emf}$$

Because we know that $i = \frac{V}{R}$, $\frac{K^2}{b}$ is a resistor. If we go back to lab3 - Oscillator, we'll find that $i_m = C \dot{V_{emf}}$ can be mathed around to $V = \frac{1}{C} \int i \, dt$ which is totally the capacitor formula. Holy squids! This is an RC circuit...which means $\tau = RC$ is true!

$$\tau = RC$$

$$R = \frac{K^2}{b}$$

$$C = \frac{I}{K^2}$$

$$\tau = \frac{K^2}{b} \cdot \frac{I}{K^2} = \frac{I}{b}$$

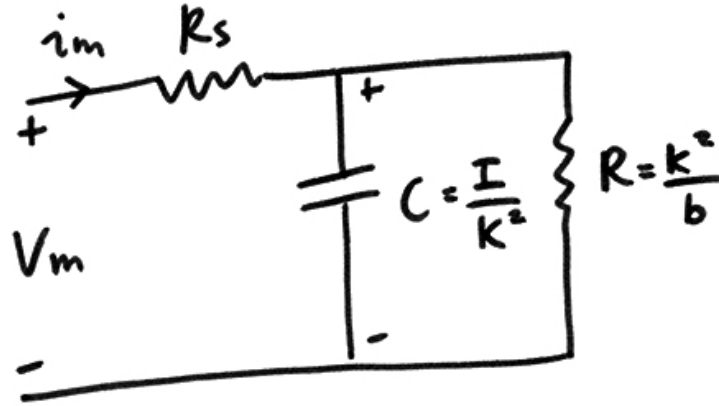


Figure 3: oooooo, ahhhhh

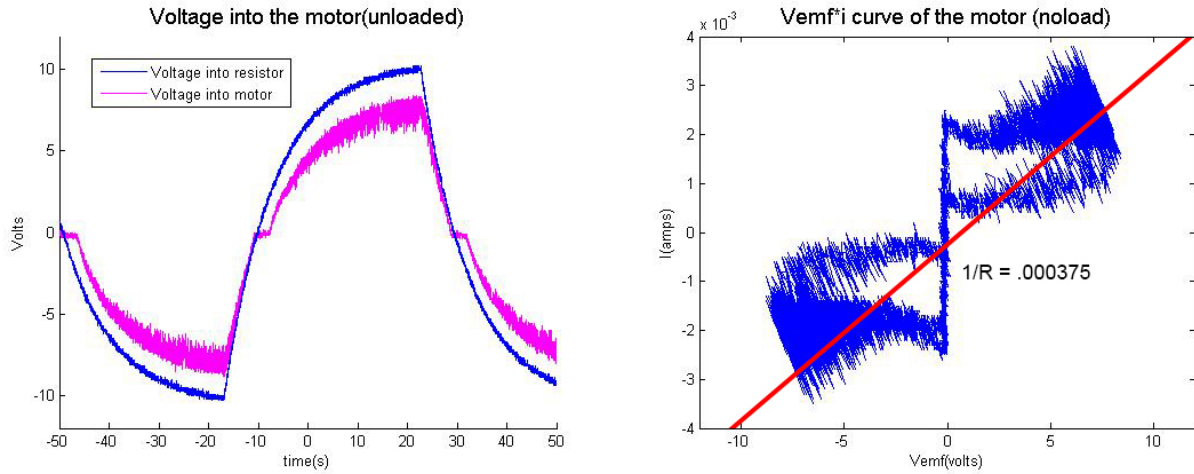


Figure 4: We find the resistance of resistor by taking the slope

Calculating b_{noload} and I_{noload} .

$$R = \frac{K^2}{b} = 2666\Omega$$

$$K = 0.26V \cdot s$$

$$b_{noload} = 2.53 \times 10^{-5}$$

$$\tau_{noload} = 0.484 = \frac{I_{noload}}{b_{noload}}$$

$$I_{noload} = 1.23 \times 10^{-5} kg \cdot m^2$$

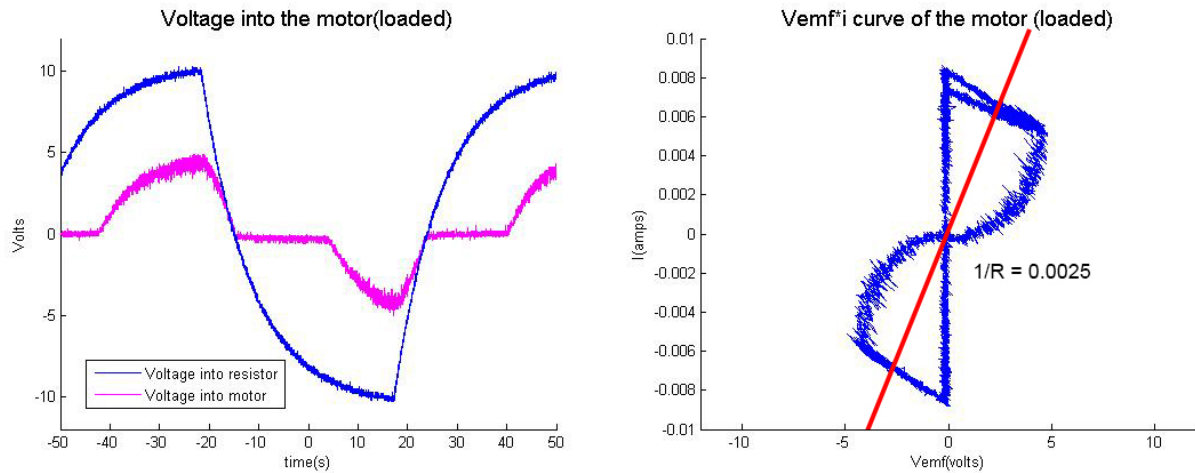


Figure 5: Dayum this motor be loaded.

Calculating b_{loaded} and I_{loaded} .

$$R = \frac{K^2}{b} = 400\Omega$$

$$K = 0.26V \cdot s$$

$$b_{loaded} = 1.69 \times 10^{-4}$$

$$\tau_{loaded} = 5.372 = \frac{I_{loaded}}{b_{loaded}}$$

$$I_{loaded} = 9.08 \times 10^{-4} kg \cdot m^2$$

Inertia is greater when there's a huge chunk of delrin on my motor...sounds pretty reasonable.